

810803088

P1




```
1 module DLR(input D,clk,Re , output Q);
2   wire QM, QbarM , Qbar;
3   nand(QM , D , clk); //if we want to reset while clock is on we can add a Re here which is overwrite
4   nand(QbarM , QM , clk);
5   nand(Qbar , Q , QbarM , Re);
6   nand(Q,QM,Qbar);
7 endmodule
```

Amirali Mokhtarian

CA 4

810803088

①

 


P2



```
1 `timescale 1ns/1ns
2 module DLR2(input D,clk,Re , output Q);
3     wire QM, QbarM , Qbar;
4     nand #8 (QM , D , clk);
5     nand #8 (QbarM , QM , clk);
6     nand #12 (Qbar , Q , QbarM , Re);
7     nand #8 (Q,QM,Qbar);
8 endmodule
```

② gates delay:

Nand1:

 

to 0 delay:

$$4 + 4 = 8 = \text{to 1 \& to 0 delay}$$

3-input Nand1:


$$4 + 4 + 4 = 12ns \text{ to 1, to 0 delay } \checkmark$$

P3

```

1 `timescale 1ns/1ns
2 module DTB();
3     reg D,Re,clk;
4     wire Q;
5     DLR2 DT(.D(D), .Re(Re), .clk(clk), .Q(Q));
6
7     initial begin
8         #50;
9         D=1'b1; clk=1'b0;
10        Re=1'b0; #50;
11
12        Re=1'b1; clk=1'b1; #50;
13
14        clk=1'b0; D=1'b0; #50;
15        clk=1'b1; #50;
16
17        //glitch
18        D=1'b1; #10;
19        clk=1'b0; #30;
20        clk=1'b1; #25;
21
22        //trancparency
23        D=1'b0; #50;
24        D=1'b1; #50;
25
26        $finish;
27    end
28 endmodule

```

 


P4



```
1 module DLR_inz(input D,clk,Re,inz , output Q);
2   wire QM, QbarM , Qbar;
3   wire D_syn, inzBAR;
4
5   not #6 (inzBAR , inz);
6
7   and #14 (D_syn , inzBAR , D);
8   nand #8 (QM , D_syn , clk);
9   nand #8 (QbarM , QM , clk);
10  nand #12(Qbar , Q , QbarM , Re);
11  nand #8 (Q,QM,Qbar);
12 endmodule
```

④

 

delay of inverter: 6

and delay: $\Rightarrow D \rightarrow \Delta \rightarrow \equiv \Rightarrow D$


$$6 + 8 = \boxed{14ns}$$

P5

```

1 module MSRR8(input clk, Re, inz, sIn , input [1:0]mode , output [7:0]Q);
2     reg [7:0] D_in;
3     generate
4         genvar i;
5         for(i=0 ; i<8 ; i=i+1) begin
6             always @(*) begin
7                 case (mode)
8
9                     2'b00: D_in[i]=Q[i];
10
11                     2'b01: begin
12                         if(i==7)
13                             D_in[i]=sIn;
14                         else
15                             D_in[i]=Q[i+1];
16                         end
17
18                     2'b10: begin
19                         if(i==7)
20                             D_in[i]=Q[0];
21                         else
22                             D_in[i]=Q[i+1];
23                         end
24
25                     2'b11: begin
26                         if(i==7 || i==6)
27                             D_in[i]=sIn;
28                         else
29                             D_in[i]=Q[i+2];
30                         end
31
32                     endcase
33                 end
34
35                 DLR_inz latch_i(.D(D_in[i]), .clk(clk) , .Re(Re) , .inz(inz), .Q(Q[i]));
36             end
37         endgenerate
38     endmodule


```

 

 6) It doesn't work as expected because this MSRR is made by latches which are transparent (more detail is in uploaded pdf report.)

P6

```
1  `timescale 1ns/1ns
2  module MSRR8_TB();
3      reg clk, Re, inz;
4      reg [1:0] mode;
5      reg sIn;
6      wire [7:0] Q;
7
8      MSRR8 dut(.clk(clk), .Re(Re), .inz(inz), .sIn(sIn), .mode(mode), .Q(Q));
9
10     initial begin
11         clk = 1'b0;
12         forever begin
13             clk = ~clk; #50;
14         end
15     end
16
17     initial begin
18         sIn = 1'b1;
19         mode = 2'b00;
20         Re=1'b1;
21         inz=1'b0;
22
23         mode = 2'b00; #200;
24         mode = 2'b01; #200;
25         mode = 2'b10; #200;
26         mode = 2'b11; #200;
27
28         mode = 2'b00;
29         Re = 1'b0; #200;
30         Re = 1'b1; #200;
31         inz = 1'b1; #400;
32         inz = 1'b0; #200;
33
34         $finish;
35     end
36 endmodule
37
```




Our MSRR8 is built using master–slave D latches, not edge-triggered D flip-flops. Because latches are transparent when their clock input is active, the internal value can propagate through multiple stages during the same clock level. This transparency is the main cause of unexpected behavior.

P7




```
1 module DLR(input D,clk,Re , output Q);
2     wire QM, QbarM , Qbar;
3     nand(QM , D , clk);
4     nand(QbarM , QM , clk);
5     nand(Qbar , Q , QbarM , Re);
6     nand(Q,QM,Qbar);
7 endmodule
8
9 module DFF(input D , clk , inz , Re , output Q);
10     wire D_syn , inzBAR , clkBAR , Q1;
11     not(inzBAR , inz);
12     and(D_syn , D , inzBAR);
13
14     DLR dlr1(D_syn , clk , Re , Q1);
15     not(clkBAR , clk);
16     DLR dlr2(Q1 , clkBAR , Re , Q);
17 endmodule
18
19
```

 



```
1  `timescale 1ns/1ns
2  module TB7();
3      reg D,inz,clk,Re;
4      wire Q;
5      DFF dfftb(.D(D) , .inz(inz) , .Re(Re) , .clk(clk) , .Q(Q));
6      initial begin
7          #50;
8          {D,inz,clk,Re}=4'b1011; #50;
9          {D,inz,clk,Re}=4'b1001; #50;
10         {D,inz,clk,Re}=4'b0011; #50;
11         {D,inz,clk,Re}=4'b0001; #50;
12         {D,inz,clk,Re}=4'b1011; #50;
13         {D,inz,clk,Re}=4'b1001; #50;
14
15         {D,inz,clk,Re}=4'b1111; #50;
16         {D,inz,clk,Re}=4'b1101; #50;
17
18         {D,inz,clk,Re}=4'b1011; #50;
19         {D,inz,clk,Re}=4'b1001; #50;
20
21         {D,inz,clk,Re}=4'b1111; #50;
22         {D,inz,clk,Re}=4'b1001; #50; //inz=0 so it looks like it shouldn't reset
23         //but the value 1 doesn't propagate yet because of edge triggering
24
25         //Re checking:
26         {D,inz,clk,Re}=4'b1011; #50;
27         {D,inz,clk,Re}=4'b1001; #50;
28         {D,inz,clk,Re}=4'b1000; #50;
29     end
30
31 endmodule
```


 


```
1  module MSRR8_FF (input clk, Re, inz, sIn, input [1:0]mode , output [7:0]Q);
2      reg [7:0]D_in;
3      generate
4          genvar i;
5          for(i=0 ; i<8 ; i=i+1) begin
6              always @(sIn, clk, Q) begin
7                  case (mode)
8
9                      2'b00: D_in[i]=Q[i];
10
11                      2'b01: begin
12                          if(i==7)
13                              D_in[i]=sIn;
14                          else
15                              D_in[i]=Q[i+1];
16                      end
17
18                      2'b10: begin
19                          if(i==7)
20                              D_in[i]=Q[0];
21                          else
22                              D_in[i]=Q[i+1];
23                      end
24
25                      2'b11: begin
26                          if(i==7 || i==6)
27                              D_in[i]=sIn;
28                          else
29                              D_in[i]=Q[i+2];
30                      end
31                  endcase
32              end
33              DFF DD(.D(D_in[i]), .clk(clk) , .Re(Re) , .inz(inz), .Q(Q[i]));
34          end
35      endgenerate
36  endmodule
```



```
1  `timescale 1ns/1ns
2  module MSRR8_DFF();
3      reg clk, Re, inz;
4      reg [1:0] mode;
5      reg sIn;
6      wire [7:0] Q;
7
8      MSRR8_FF MSTB(.clk(clk), .Re(Re), .inz(inz), .sIn(sIn), .mode(mode), .Q(Q));
9
10     initial begin
11         clk = 1'b0;
12         forever begin
13             clk = ~clk; #50;
14         end
15     end
16
17     initial begin
18         mode = 2'b00;
19         sIn = 1'b0;
20         inz = 1'b0;
21         Re = 1'b1;
22         #100;
23
24         Re = 1'b0;
25         #100;
26
27         Re=1'b1; #50;
28         sIn=1'b1; mode=2'b01; #800;
29         sIn=1'b0;
30         Re=1'b0; #100;
31         Re=1'b1;
32         sIn=1; #100;
33
34         mode=2'b10; #850;
35
36         sIn=1'b0; #100;
37         mode=2'b11; #800;
38
39         sIn=1'b1;
40         mode = 2'b01; #800;
41         inz=1'b1; #100;
42         $finish;
43     end
44 endmodule
45
```

Waveform of 8

  

P9


```

1  module DFF_al(input clk, Re, inz , D , output reg Q);
2      reg QM;
3      always @(posedge clk) begin
4          QM = D;
5      end
6
7      always @(negedge clk) begin
8
9          if(Re==1'b0)begin
10             Q<=1'b0;
11         end
12
13         else begin
14             if(inz)
15                 Q<=1'b0;
16             else
17                 Q<=QM;
18         end
19     end
20
21     assign Q = Q ? Re : 1'b0;
22
23 endmodule

```





```
1 `timescale 1ns/1ns
2
3 module DFF_alTB();
4     reg clk, D, Re , inz;
5     wire Q;
6     DFF_al DF(.clk(clk), .Re(Re), .inz(inz) , .D(D) , .Q(Q));
7     initial begin
8         D=1'b0; inz=1'b0; Re=1'b1; clk=1'b1; #50
9
10        clk=1'b0; #50;
11        D=1'b1; clk=1'b1; #50
12        clk=1'b0; #50;
13
14        Re=1'b0; #50;
15        Re=1'b1; #50;
16
17        clk=1'b1; D=1'b1; #50;
18        clk=1'b0; #50;
19
20        clk=1'b1; inz=1'b1; #50;
21        clk=1'b0; #50;
22
23        $finish;
24
25    end
26 endmodule
```

 

```
1  module MSRR8(input clk, Re, inz, sIn , input [1:0]mode , output [7:0]Q);
2      reg [7:0] D_in;
3      generate
4          genvar i;
5          for(i=0 ; i<8 ; i=i+1) begin
6              always @(*) begin
7                  case (mode)
8
9                      2'b00: D_in[i]=Q[i];
10
11                      2'b01: begin
12                          if(i==7)
13                              D_in[i]=sIn;
14                          else
15                              D_in[i]=Q[i+1];
16                      end
17
18                      2'b10: begin
19                          if(i==7)
20                              D_in[i]=Q[0];
21                          else
22                              D_in[i]=Q[i+1];
23                      end
24
25                      2'b11: begin
26                          if(i==7 || i==6)
27                              D_in[i]=sIn;
28                          else
29                              D_in[i]=Q[i+2];
30                      end
31
32                  endcase
33              end
34
35              DLR_inz latch_i(.D(D_in[i]), .clk(clk) , .Re(Re) , .inz(inz), .Q(Q[i]));
36          end
37      endgenerate
38  endmodule
```



```
1 `timescale 1ns/1ns
2 module MSRR8_comp();
3     reg clk, Re, inz;
4     reg [1:0] mode;
5     reg sIn;
6     wire [7:0] Q,Qalways;
7
8     MSRR8_FF MSTB(.clk(clk), .Re(Re), .inz(inz), .sIn(sIn), .mode(mode), .Q(Q));
9     MSRR8_alw MALW(.clk(clk), .Re(Re), .inz(inz), .sIn(sIn), .mode(mode), .Q(Qalways));
10
11     initial begin
12         clk = 1'b0;
13         forever begin
14             clk = ~clk; #50;
15         end
16     end
17
18     initial begin
19         mode = 2'b00;
20         sIn = 1'b0;
21         inz = 1'b0;
22         Re = 1'b1;
23         #100;
24
25         Re = 1'b0;
26         #100;
27
28         Re=1'b1; #50;
29         sIn=1'b1; mode=2'b01; #800;
30         sIn=1'b0;
31         Re=1'b0; #100;
32         Re=1'b1;
33         sIn=1; #100;
34
35         mode=2'b10; #850;
36
37         sIn=1'b0; #100;
38         mode=2'b11; #800;
39
40         sIn=1'b1;
41         mode = 2'b01; #800;
42         inz=1'b1; #100;
43         $finish;
44     end
45 endmodule
46
```

  

They aren't match exactly because In the gate-level circuit, signals pass through several NAND gates, causing small timing shifts or brief glitches that affect the output. The always-based register has no delays and produces clean, synchronous transitions. The main point is that always_based is an ideal MSRR(with no delays) and it's functionally correct(not in a real world).