


## Problem 1

Pre\_synthesize:

```
1  module ALU1(input [15:0]inA,inB , input[2:0]opc , input inC , output reg [15:0]outW , output zer,neg);
2
3      always @(opc,inA,inB,inC) begin
4          outW=16'b0;
5          case(opc)
6              3'b000: outW= inA + inB +inC;
7              3'b001: outW= inA + 16'd1;
8              3'b010: outW = ($signed(inA) >= $signed(inB)) ? inA : inB; //use signed for negatives
9              3'b011: outW = inA + (inB >>> 1); //right shift to divide by 2
10             3'b100: outW= inA & inB;
11             3'b101: outW= inA | inB;
12             3'b110: outW= ~inA;
13             3'b111: outW = 16'b0;
14
15             default:
16                 outW = 16'bx;
17         endcase
18     end
19
20     assign zer = (outW==16'b0);
21     assign neg = outW[15]; //MSB
22
23 endmodule
```

By synthesizing the code with Yosys we will get post\_synthesized code (which include the library gates). Post\_synthesizedd file is uploaded in the Zip file.

problem-1 diagram ?

 

## Gates used for ALU1.v


```
=== ALU1 ===  
  
Number of wires:           494  
Number of wire bits:       541  
Number of public wires:    7  
Number of public wire bits: 54  
Number of memories:        0  
Number of memory bits:     0  
Number of processes:       0  
Number of cells:           504  
  $_AND_                   51  
  $_AOI3_                   60  
  $_AOI4_                    3  
  $_MUX_                    30  
  $_NAND_                   33  
  $_NOR_                    69  
  $_NOT_                    77  
  $_OAI3_                   59  
  $_OAI4_                   18  
  $_OR_                     25  
  $_XNOR_                   58  
  $_XOR_                    21
```

## Gates used for ALU1\_synth.v (library gates)

```
=== ALU1 ===  
  
Number of wires:           1314  
Number of wire bits:       1361  
Number of public wires:    7  
Number of public wire bits: 54  
Number of memories:        0  
Number of memory bits:     0  
Number of processes:       0  
Number of cells:           784  
  NAND                      208  
  NOR                      443  
  NOT                      133
```

Gate count is higher in the synthesized version because the library only includes limited primitive cells.

 Here is the waveform of the test bench that I put at the end of report, to compare part a and c (W and W\_post)



As we can see here the outputs match exactly. The only difference is delay, because library cells have propagation delays. Behavioral simulation is faster and has no delay but gate-level simulation is slower and includes realistic propagation delay.

## Problem 2

Pre\_synthesizes:

```
1  module minimal_ALU(input [15:0]inA,inB , input[2:0]opc , input inC , output reg [15:0]outW , output zer,neg);
2
3      wire [15:0] add_inB =
4      (opc==3'b000) ? inB :
5      (opc==3'b001) ? 16'd1 :
6      (opc==3'b010) ? ~inB : //A+~B = A-B
7      (inB>>>1);
8
9      wire add_inC =
10     (opc==3'b000) ? inC :
11     (opc==3'b010) ? 1'b1 : //for 2's complement of B
12     1'b0;
13
14     wire [15:0] add_out = inA + add_inB + add_inC;
15
16     always @(opc,inA,inB,inC) begin
17         outW=16'b0;
18         case(opc)
19
20             3'b010: outW = (add_out[15]==0) ? inA : inB;
21
22             3'b100: outW= inA & inB;
23             3'b101: outW= inA | inB;
24             3'b110: outW= ~inA;
25             3'b111: outW = 16'b0;
26             default: outW = add_out;
27         endcase
28     end
29
30     assign zer = (outW==16'b0);
31     assign neg = outW[15]; //MSB
32
33 endmodule
```

In this version I share one adder for first four opcodes. For each of these opcodes, I only change the inputs to the adder (add\_inB and add\_inC), so the ALU can perform different operations with the same hardware.

add\_inB, add\_inC, and add\_out choose the correct inputs. This reduces the number of gates. Therefore, we must have fewer amount of gates in this case rather than the first problem.


## Gates used for minimal\_ALU.v

```
=== minimal_ALU ===  
  
Number of wires:          289  
Number of wire bits:      336  
Number of public wires:   7  
Number of public wire bits: 54  
Number of memories:       0  
Number of memory bits:    0  
Number of processes:      0  
Number of cells:          299  
  $_AND_                   20  
  $_AOI3_                   29  
  $_AOI4_                   14  
  $_MUX_                    49  
  $_NAND_                   10  
  $_NOR_                    41  
  $_NOT_                    45  
  $_OAI3_                   27  
  $_OAI4_                   16  
  $_OR_                    16  
  $_XNOR_                   23  
  $_XOR_                    9
```
 
## Gates used for minimalALU\_synth.v

```
=== minimal_ALU ===  
  
Number of wires:          947  
Number of wire bits:      994  
Number of public wires:   7  
Number of public wire bits: 54  
Number of memories:       0  
Number of memory bits:    0  
Number of processes:      0  
Number of cells:          622  
  NAND                     210  
  NOR                      306  
  NOT                      106
```

Obviously the post\_synthesized one has more gates because we have limited available gates in our library.



Just like the first problem the post\_synthesizes outputs have delay.


The test bench of 2 problems:

```

1 `timescale 1ns/1ns
2 module ALU_TB();
3     reg[15:0] A, B;
4     reg C;
5     reg [2:0]opc;
6     wire [15:0]W,W_post;
7     wire [15:0]Wmin,Wmin_post;
8     wire zer,neg,zer_post,neg_post;
9     wire zermin,negmin,zermin_post,negmin_post;
10
11     ALU1 ATB1(.inA(A), .inB(B), .opc(opc), .inC(C), .outW(W), .zer(zer), .neg(neg));
12     ALU1_synth ATB1_synth(.inA(A), .inB(B), .opc(opc), .inC(C), .outW(W_post), .zer(zer_post), .neg(neg_post));
13
14     minimal_ALU AMTB(.inA(A), .inB(B), .opc(opc), .inC(C), .outW(Wmin), .zer(zermin), .neg(negmin));
15     minimalALU_synth AMTB_synth(.inA(A), .inB(B), .opc(opc), .inC(C), .outW(Wmin_post), .zer(zermin_post), .neg(negmin_post));
16
17     integer i;
18     initial begin
19         A=16'b0 ; B=16'b0 ; C=1'b0 ; opc=3'b0; #200;
20
21         A = 16'b11111111111111110 ; B=16'd3; #200;
22
23         for(i=0 ; i<8 ; i=i+1)begin
24             opc=i; #200;
25         end
26
27         repeat(10)begin
28             A = $random();
29             B = $random();
30             C = $random();
31             opc = $random();
32             #200;
33         end
34         $stop;
35     end
36 endmodule

```

Problem 2 diagram :

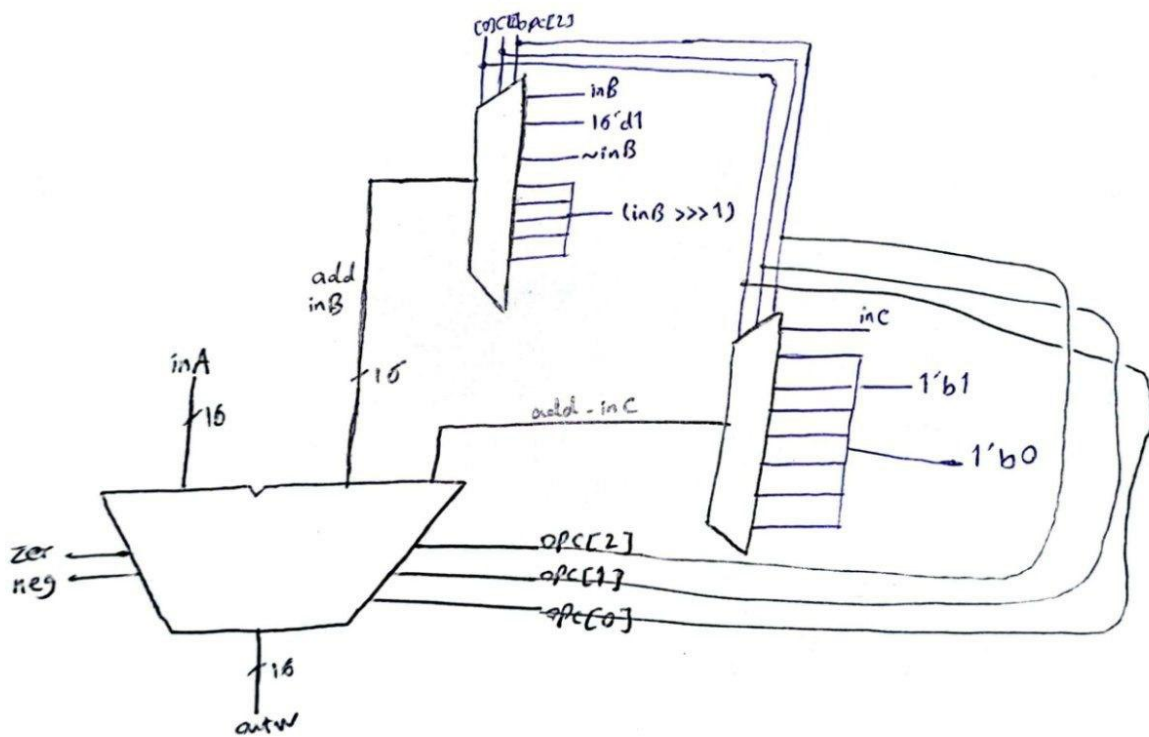

for 010 opcode the most significant bit of `add_out` must be connected to a comparator and the output of it should connect to a selector (to choose between A and B)

### Problem 3:

In both designs, the outputs are similar but their structural code has delay because the synthesized netlists use real library cells with non zero propagation time. The behavioral ALU synthesizes have more hardware because each opcode is implemented separately, while the structural one has less hardware because it just uses a single adder for first opcodes.

Shared data path for the second problem makes its critical path longer than the first one. Therefore, the hardware\_oriented design is smaller but slower than behavioral ALU.